



Worcester Polytechnic Institute
Electrical and Computer Engineering Department

Test and Testable Design

Online Offering – Spring 2024

Homework 1: Logic design, Verilog modeling and testbenches

Due Date: February 04

Description:

The selection sort algorithm is a simple comparison-based sorting algorithm. It works by dividing the input into two parts: the subarray of sorted elements and the subarray of unsorted elements. In each iteration, the algorithm selects the smallest (or largest, depending on the sorting order) element from the unsorted subarray and swaps it with the first element of the unsorted subarray. This process continues until the entire array becomes sorted. At each step, the smallest (or largest) element is identified and "selected" to be placed in its correct position. This selection process gives the algorithm its name. The selection sort algorithm has an average and worst-case time complexity of $O(n^2)$, where n is the number of elements in the array. It is not suitable for large datasets since its time complexity grows quadratically. However, it has the advantage of being simple to understand and implement.

For more information you can use following sources:

<http://www.geeksforgeeks.org/selection-sort/>

SSC Design:

You are to design a sorter circuit that uses the selection sort algorithm to sort a block of 256 16-bit unsigned words in an ascending order. Figure 1 shows the top-view specification of the selection sorter circuit (SSC). Data collected becomes available in a memory buffer between the wrapper and the SSC. The memory buffer has read and write signals for its read and write operations. A wrapper sitting next to our processing element (PE), sorter circuit, is responsible for collecting data and informing our PE that data collection is completed and sorting can start. This is done by the wrapper issuing a complete positive pulse on the *start* signal. When sorting is completed, the SSC issues a complete positive pulse on its *done* signal.

The Datapath and Controller of the SSC are illustrated in Figure 2 and Figure 3, respectively. After achieving a positive pulse on the *start* signal, two counters and all registers are reset to zero. Once a complete pulse is detected on the *start* signal, the sorting procedure begins and the value 1 is loaded into counter2. Counter1 is addressing the last word of the sorted part of the memory block. At this state it is addressing the first word of the memory buffer. The data and its address are saved in the Min_reg and Minaddr_reg, respectively. In each cycle, counter2 increments by one, and the corresponding data is obtained from the memory buffer. This data is then compared with the data of Min_reg. If a smaller data value is found, it is saved along with its address. This procedure repeats until the value of counter2 reaches 255. At this point, the minimum value from the unsorted section has been identified and needs to be moved to the sorted portion. The movement of the minimum value occurs in three update stages: update0, update1, and update2. During these stages, the minimum value is replaced with the first member of the unsorted section, whose address is determined by the value of counter1 that is incremented by one.

This process continues until the value of counter1 reaches 255, indicating that all the data has been sorted.

Assignment:

You are provided with the design of SSC. You are to:

1. Show Verilog description of the components of the datapath and then enclose them in the complete datapath.
2. Show Verilog description of the controller according to the provided FSM, using Huffman modeling style.
3. In a top-level Sorter Circuit architecture, put the datapath and controller of the circuit together.
4. Generate an appropriate testbench to test your design (Control the duration of running a testbench, using “\$stop or \$finish”).

***For initializing the memory buffer use the given *data.txt* file (Use \$readmemb for reading text IO).

Attention:

This homework covers “Review – Logic Design at RT Level” and “Chapter 2 – Verilog HDL for design and test” modules on Canvas.

Deliverables:

All Verilog codes and a complete report containing all parts of the assignment. Make sure that your deliverable follows all mentioned rules in the assignment part of "*ECE5724 - Comprehensive Format Syllabus.pdf*" file. The file has been posted on Canvas.

 


Figure 1: Top view of Selection Sorter Circuit

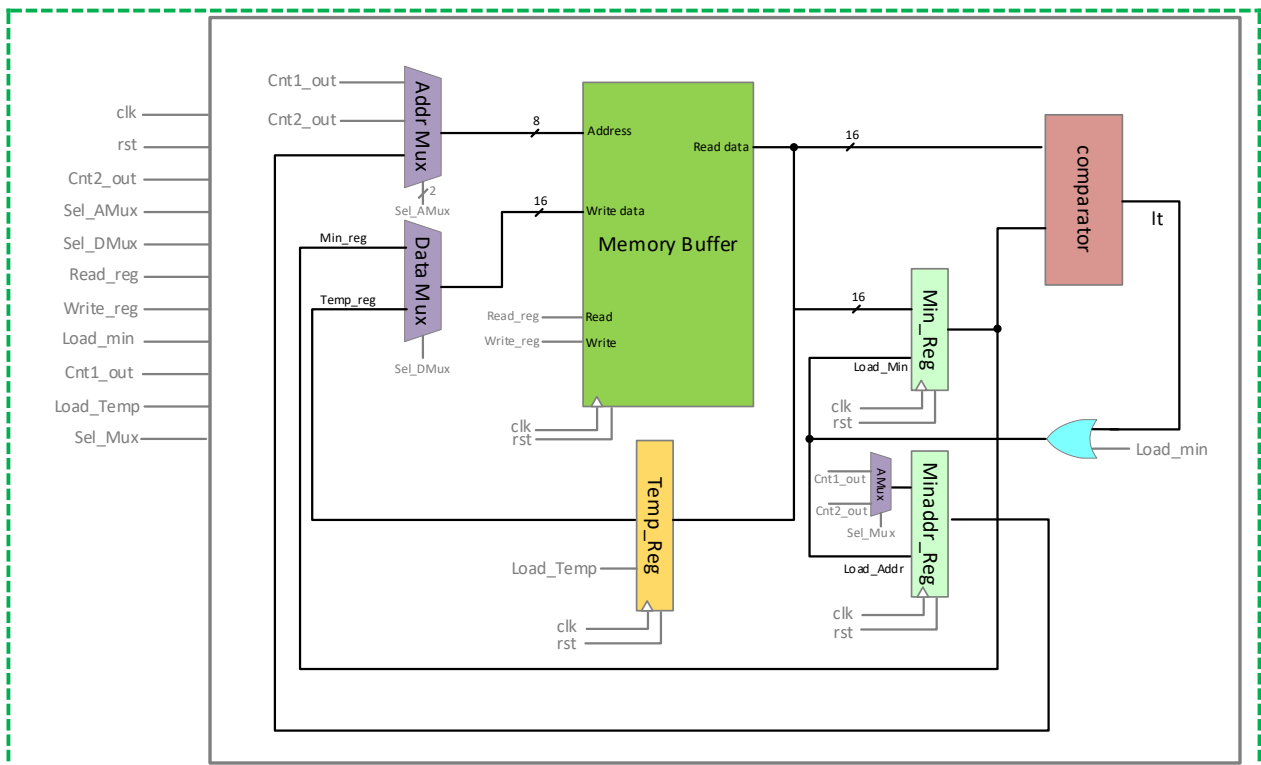


Figure 2: Selection Sorter Circuit Datapath

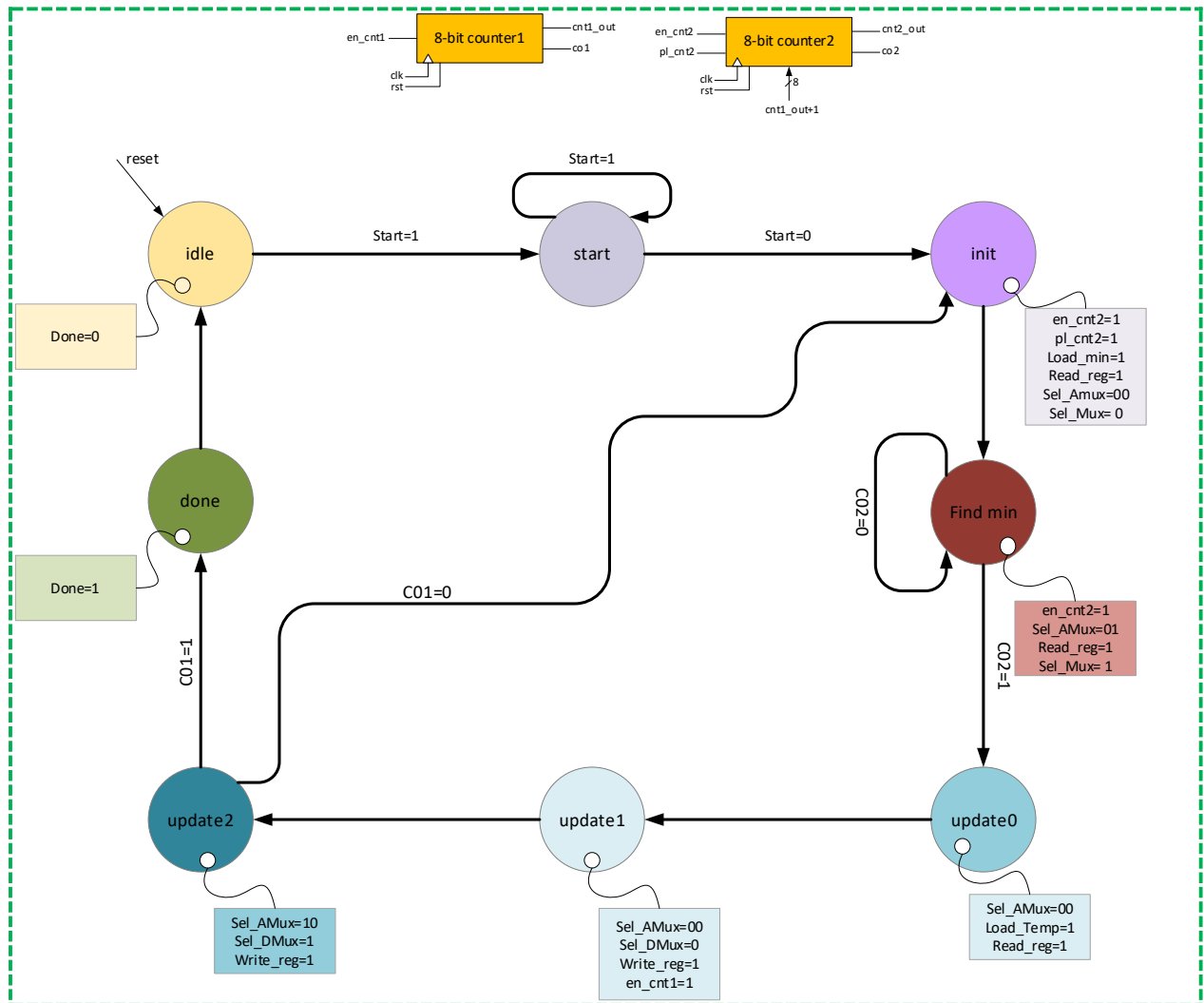


Figure 3: Selection Sorter Circuit Controller